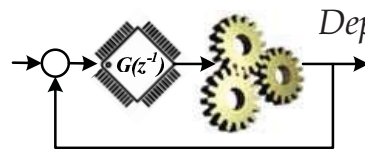


Chapter 7

ATmega328 Interfacing with High Voltage / Current

Assoc. Professor Dr. Rosbi bin Mamat

rosbi@fke.utm.my



Dept. of Control & Mechatronics Engineering

Faculty of Electrical Engineering

Universiti Teknologi Malaysia


7.1 Isolation

- When high current or high voltage devices are connected to a μC system, **Isolation** must be made between high voltage/current devices & μC system to avoid high voltage/current damages μC or human!.
- **Optoisolator / Optocoupler**
 - Optoisolator uses LED (as transmitter) & opto detector (as receiver) to send signal through light. LED is connected to output port of μC & photo-transistor output is connected to high voltage/current device.
 - \therefore LED & opto detector are separated by insulated air, **isolation** between μC & devices is achieved.

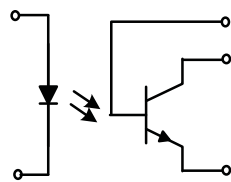
7.2 Isolation – Optoisolator

● Optoisolator / Optocoupler


- Optoisolator is useful to control devices which are slightly remote from μC system & devices which have separate power supply from μC .
- Sample types of optoisolator:



Transistor Output
(4N26)

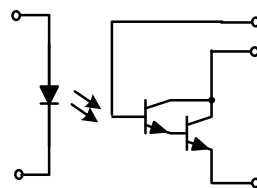

Darlington Output
(MOC119)

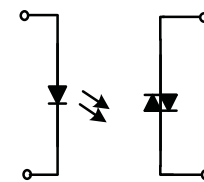


Triac Output
(MOC3011)

7.3 Isolation – Electromagnetic Relay

- **Electromagnetic Relay** can be used to control high voltage/current devices.

Structure of a relay:

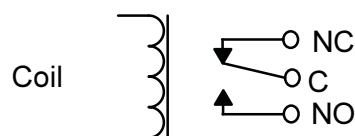


C - common terminal
NC - normally closed terminal
NO - normally opened terminal

- Relay can control devices with DC or AC voltages.
 Must choose suitable relay with specific devices.

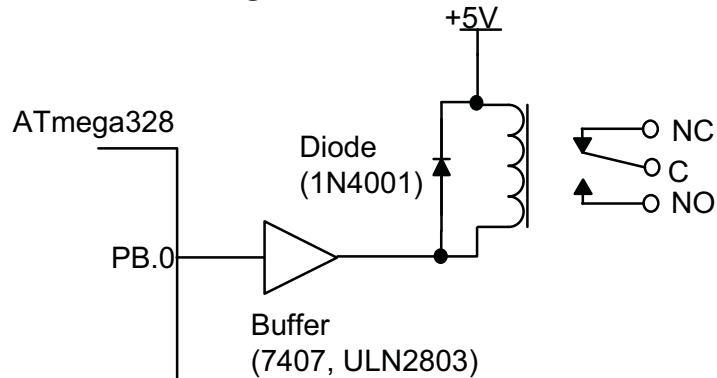7.3 Isolation – Electromagnetic Relay

● Electromagnetic Relay

- For relays with low coil voltage (≤ 5 volts) & small current, the following circuit can be used:




- The diode is used to avoid negative voltage induced in the coil from damaging the buffer & ATmega328.

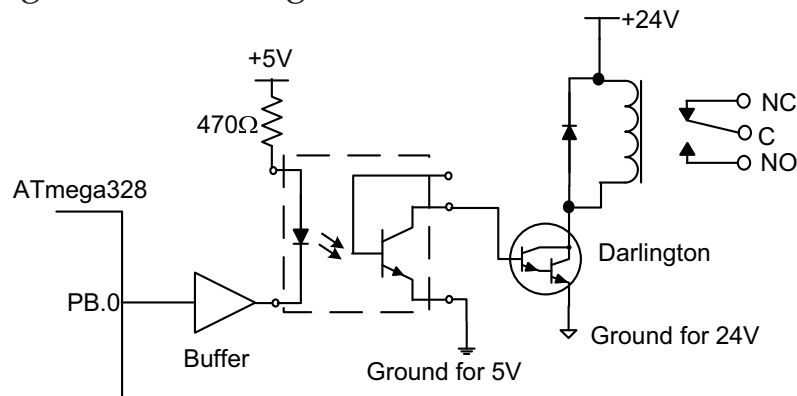7.3 Isolation – Electromagnetic Relay


● Electromagnetic Relay

- When a relay with high voltage (> 5 volts) & high current coil, or when the relay output need to be connected to AC devices, an optoisolator can be used with a relay. For example, for a relay with +24V coil voltage, the following circuit can be used:



7.4 Interfacing With DC Motor

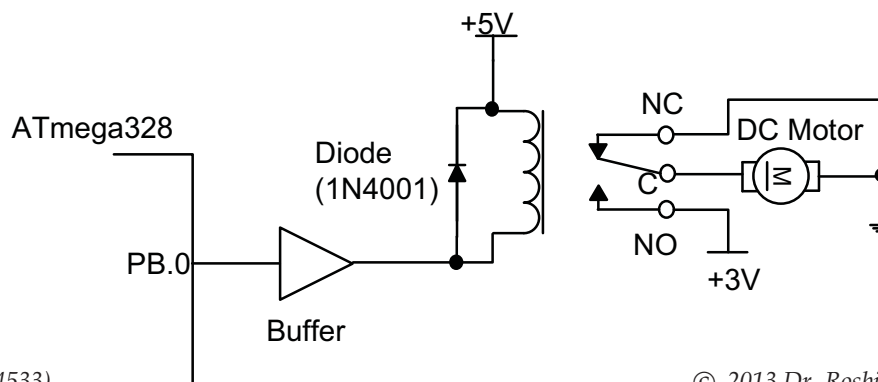- **Example:** Interfacing a small DC motor (+3V, 500mA) to ATmega328.
- **Solution:** The DC motor **SHOULD NOT** be connected directly to ATmega328 because the 500mA current can burn the ATmega328. We can use +5V relay. When PB0='1', motor stops & When PB0='0', motor rotates (one way only!).




Microcontroller (SEL4533)

© 2013 Dr. Rosbi Mamat – p.6/17

7.4 Interfacing With DC Motor

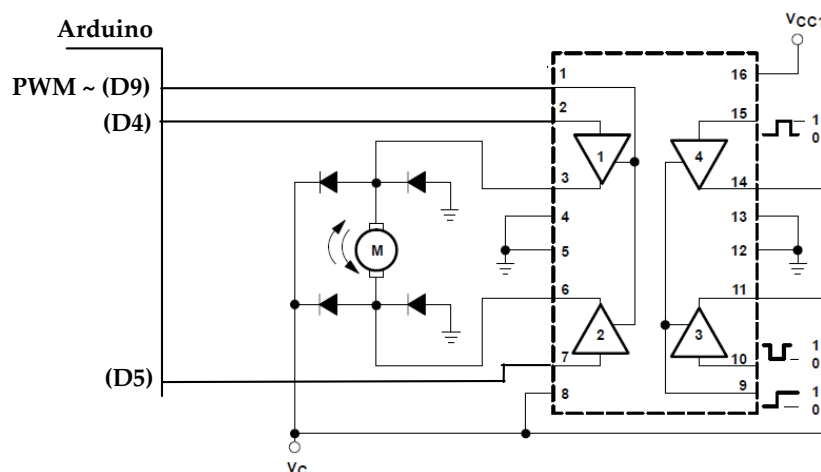- **Example:** Interfacing a small DC motor (+3V, 500mA) to ATmega328.
- **Solution:** Use a motor driver IC such as L293. Direction of rotation is set by D4 & D5. Motor speed is controlled by Pulse Width Modulation (PWM) on pin D9.



Microcontroller (SEL4533)

© 2013 Dr. Rosbi Mamat – p.7/17

7.4 Interfacing With DC Motor

- **Example:** Interfacing a small DC motor (+3V, 500mA) to ATmega328.
- **Solution:** Sample program in Arduino:

```


void setup() {
  pinMode(D4, OUTPUT); // D4 & D5 for motor
  pinMode(D5, OUTPUT); // direction control
  analogWrite(9, 0); // stop motor
}

void loop() {
  digitalWrite(D4, HIGH); // rotate clockwise
  digitalWrite(D5, LOW);
  analogWrite(9, 255); // full speed
  delay(10000); // wait 10 secs
  analogWrite(9, 0); // stop motor
}

```

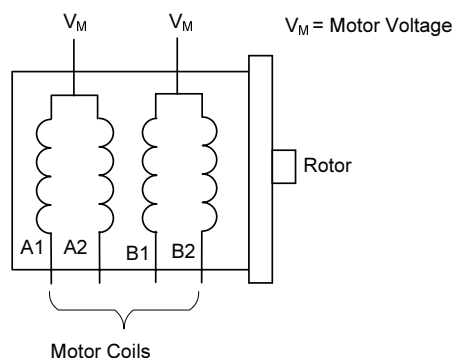7.5 Interfacing with Stepper Motor

- **Stepper motor** – a type of motor which rotates step-by-step in a specific angle.
- Common angles for each step are: 15° & 7.5° . For a stepper motor with step angle 15° , a complete rotation (360°) requires 24 steps.
- Stepper motors are used in printers, disc drives & robots.



7.5 Interfacing with Stepper Motor

- Comparison between stepper motor & DC motor:

Stepper Motor	DC Motor
Rotates in steps	Rotates continuously
Can be controlled in open-loop. Does not require sensor for position feedback	Must be controlled in closed-loop. Requires position sensor for feedback
Control software is easier to write	Complex control software

- Driving a stepper motor involves applying voltages to motor coils (A1, A2, B1 & B2) in a specific sequence.

7.5 Interfacing with Stepper Motor


- In full-step mode, the following sequence of voltages must be applied to motor coils.

Sequence	A1	A2	B1	B2	Code (Hex)
1	1	0	1	0	\$0A
2	1	0	0	1	\$09
3	0	1	0	1	\$05
4	0	1	1	0	\$04

- '1' on A1, A2, B1 & B2 means V_M Volts is applied. '0' on A1, A2, B1 & B2 means 0V is applied.

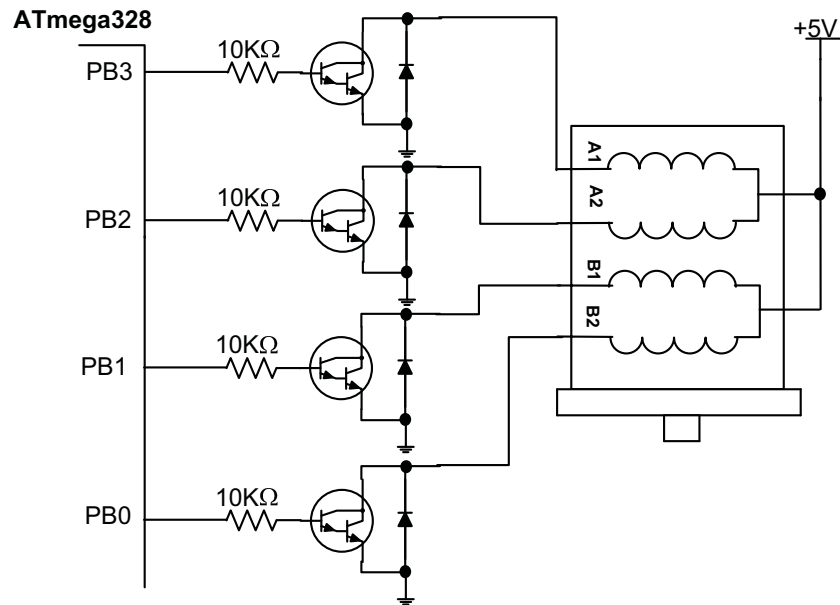7.5 Interfacing with Stepper Motor

- Direct drive circuit: Example of connecting stepper motor AIRPAX 5V with 7.5° per step.



7.5 Interfacing with Stepper Motor

- To step the motor in clock-wise direction this sequence of codes : \$0A, \$09, \$05, \$06 are repeatedly sent to Port B (lower nibble only).
- To step the motor in counter clock-wise direction this sequence of codes: \$06, \$05, \$09, \$0A are repeatedly sent to Port B.
- Normally, a delay is performed between the codes sent to allow the motor to reach steady-state & to produce rotation in a specified speed.

7.5 Interfacing with Stepper Motor

- Stepper motor driver chips e.g. SAA1027, L297/298, UCN4204B etc. are available. Advantages of using these driver chips are:
 - Simplified the interfacing circuit with μC .
 - Simplified software writing since the programmer is not required to remember the sequence of codes sent.
 - Driver chips already have the required voltage/current capability to drive stepper motor directly.

7.5 Interfacing with Stepper Motor

- **Example:** Write a program to rotate an AIRPAX stepper motor in previous slide for 60° clock-wise & then 15° counter clock-wise. This motor require 10ms to reach steady-state.
- **Solution:** To rotate 60° 8 steps are required & 15° requires 2 steps.

7.5 Interfacing with Stepper Motor

Program: Stepper motor control

```
void setup() {
  DDRB = 0x0F; // PB0-PB3 as output
}

void loop() {
  int i;

  for (i = 0; i < 2; i++) { // cw 60 degree
    PORTB = 0x0A; delay_ms(10);
    PORTB = 0x09; delay_ms(10);
    PORTB = 0x05; delay_ms(10);
    PORTB = 0x06; delay_ms(10);
  }
  // counter cw 15 degree
  PORTB = 0x05; delay_ms(10);
  PORTB = 0x09; delay_ms(10);
}
```

7.5 Interfacing with Stepper Motor

Program: Stepper motor control – using look-up table.

```
const unsigned char cw60[] = {0x0A, 0x09, 0x05, 0x06,
                              0x0A, 0x09, 0x05, 0x06};
const unsigned char ccw15[] = {0x05, 0x09};

void setup() {
  DDRB = 0x0F; // PB0-PB3 as output
}

void loop() {
  int i;

  for (i = 0; i < 8; i++) { // clock-wise 60 degree
    PORTB = cw60[i];
    delay_ms(10);
  }

  for (i = 0; i < 2; i++) { // counter cw 15 degree
    PORTB = ccw15[i];
    delay_ms(10);
  }
}
```