



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

INSPIRING CREATIVE AND INNOVATIVE MINDS


www.utm.my

Zener Diode





Zener Diode

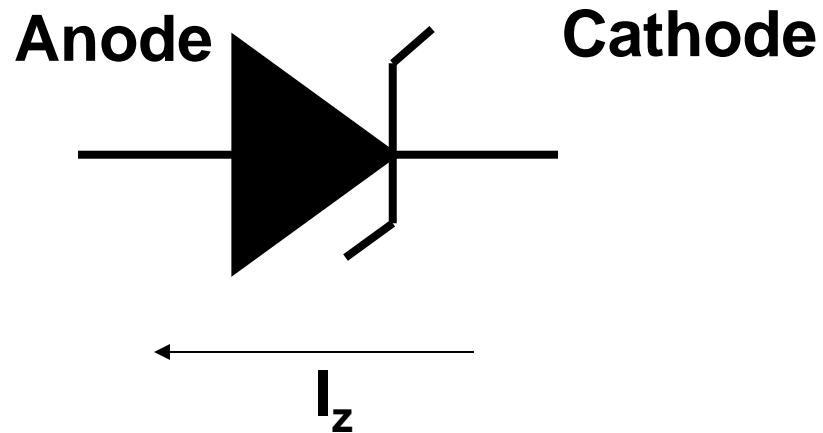


Symbol



Zener Diode

- Design to operate in reverse breakdown.
- Mainly use for voltage regulation and limiting application.
- In reverse bias, the zener diode is 'on' and the voltage across the zener diode is called Zener voltage, V_z
- In forward bias, zener diode act like the regular diode.
- Note that the direction of the current flow is different between zener and regular diode.

Zener Diode

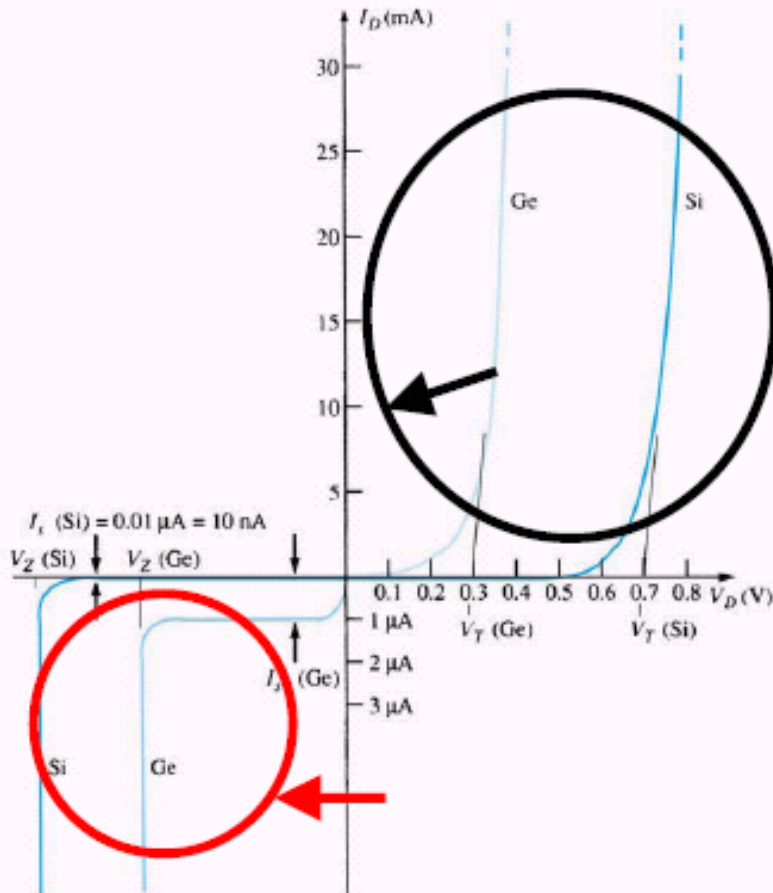


Black circle \rightarrow regular diode operating region

Red circle \rightarrow zener diode operating region


Zener Diode

www.utm.my

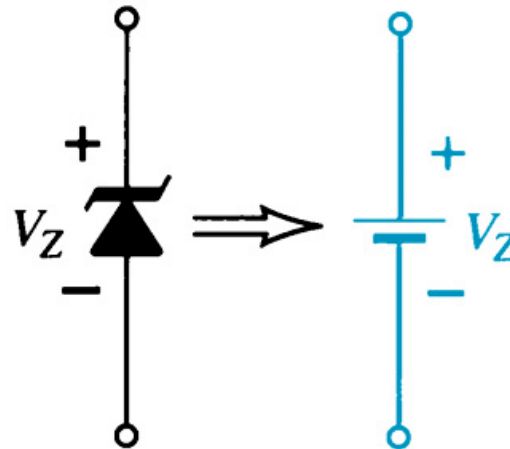

"on"

(a)

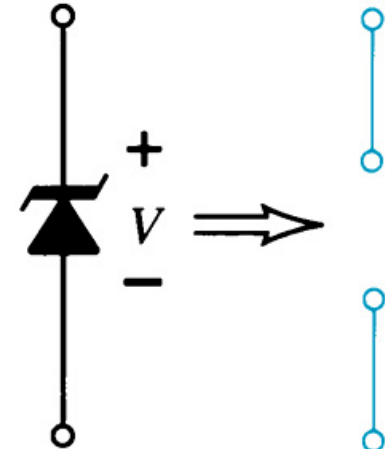

$(V_Z > V_S > 0 \text{ V})$

"off"

(b)

$V_S > V_Z$




- Three types of Zener analysis
 - Fixed V_S and R_L
 - Fixed V_S and variable R_L
 - Variable V_S and fixed R_L

- Fixed V_S and R_L

The applied dc voltage is fixed, as the load resistor.

The analysis :

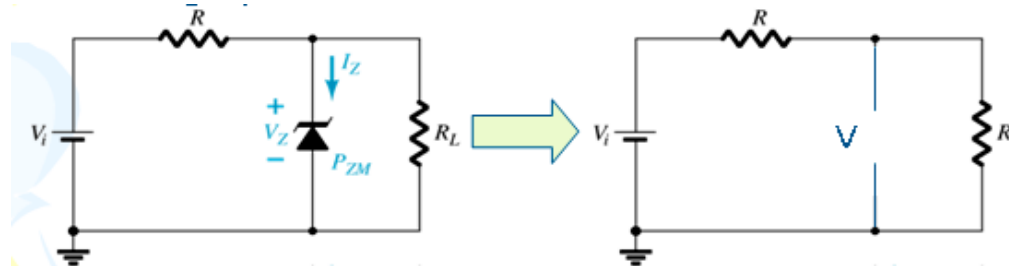1. Determine the state of the Zener diode by **removing it** from the network and **calculating the voltage** across the resulting open circuit.




Calculate the V using voltage divider rule:

$$V = V_L = \frac{R_L V_i}{R_L + R}$$

if $V \geq V_Z$, the Zener diode is on

if $V < V_Z$, the Zener diode is off

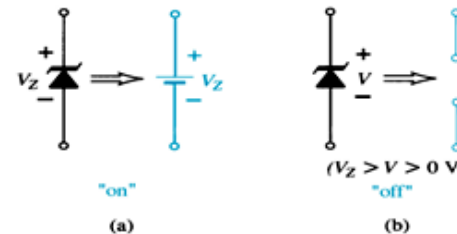



Zener Diode

2. Substitute the appropriate equivalent circuit and solve for the desired unknowns.

- For the **on state diode**, the voltages across parallel elements must be the same.

$$V_L = V_Z$$

The Zener diode current is determined by KCL:


$$I_Z = I_R - I_L$$

The power dissipated by the Zener diode is determined by:

$$P_Z = V_Z I_Z$$

- For the **off state diode**, the equivalent circuit is open-circuit.

- Fixed V_S and Variable R_L

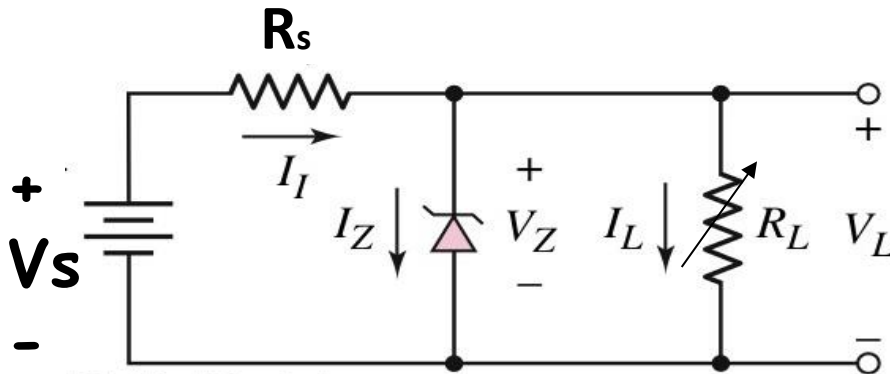

ht © The McGraw-Hill Companies, Inc.
ion required for reproduction or display.

Step 1- get the R_{Lmin} so that zener is on.

$$V_L = \frac{R_L V_S}{R_S + R_L} \longrightarrow R_{Lmin} = \frac{R_S V_Z}{V_S - V_Z}$$

- if $R_L \geq R_{Lmin}$, zener diode 'on', so that $V_L = V_Z$

Step 2: Calculate the I_Z using KCL: 2 condition

1. If R_{Lmin} , then I_{Lmax} and I_{Zmin} because of constant I_1
2. If R_{Lmax} , then I_{Lmin} and I_{Zmax}




Zener Diode

$$I_{Z \text{ min or max}} = I_{\text{constant}} - I_{L \text{ max or min}} \quad ; \text{ Izmax taken from data sheet}$$

Izmin = 0, if not given

Where $I_1 = \frac{V_S - V_Z}{R_S}$ **and** $I_{L \text{ max}} = \frac{V_Z}{R_{L \text{ min}}}$ **or** $R_{L \text{ max}} = \frac{V_Z}{I_{L \text{ min}}}$

- Variable V_S and fixed R_L

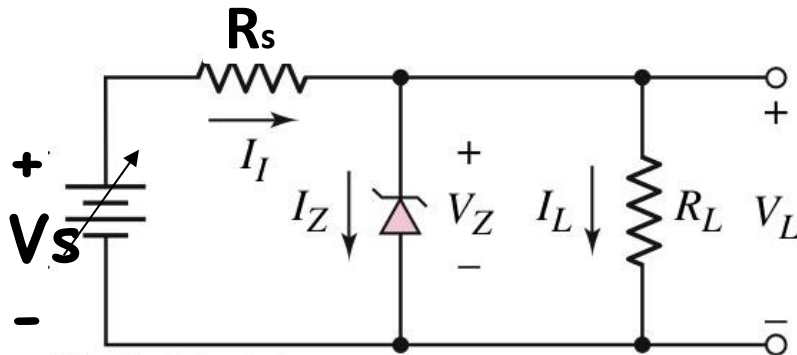

ht © The McGraw-Hill Companies, Inc.
ion required for reproduction or display.

Step 1- get the V_{Smin} so that zener is on.

$$V_L = \frac{R_L V_S}{R_S + R_L} \longrightarrow V_{Smin} = \frac{(R_L + R_S)V_Z}{R_L}$$

if $V_S \geq V_{Smin}$, zener diode will 'on', so that $V_L = V_Z$

Step 2: Calculate the I_Z using KCL: 2 condition

1. if V_{Smin} , then I_{1min} and I_{Zmin} because of constant I_L
2. if V_{Smax} , then I_{1max} and I_{Zmax}



Zener Diode

$$I_{Z \text{ min or max}} = I_{1 \text{ min or max}} - I_{L \text{ constant}} \quad ; \quad I_{Z \text{ max}} = P_{Z \text{ max}} / V_Z$$

where $I_L = \frac{V_L}{R_L}$ and $I_{1 \text{ min}} = \frac{V_{S \text{ min}} - V_Z}{R_S}$ or $V_{S \text{ max}} = I_{1 \text{ max}} R_S + V_Z$